

Marwari college Darbhanga

Subject---physics (Hons)

Class--- B.Sc. part 2

Paper---. 04 ; group----B

Topic—Amplifier(Basic Electronics)

Lecture series- 07

By:- Dr. Sony Kumari

Assistant professor

Marwari college Darbhanga

Amplifier

An amplifier is an electronic device or circuit which is used to increase the magnitude of the signal applied to its input

Amplifier is the generic term used to describe circuit which produces an increased version of its input signal. However, not all amplifier circuits are the same as they are classified according to their circuit configurations and modes of operation.

In “Electronics”, small signal amplifiers are commonly used devices as they have the ability to amplify a relatively small input signal, for example from a *Sensor* such as a photo-device, into a much larger output signal to drive a relay, lamp or loudspeaker for example.


There are many forms of electronic circuits classed as amplifiers, from Operational Amplifiers and Small Signal Amplifiers up to Large Signal and Power Amplifiers. The classification of an amplifier depends upon the size of the signal, large or small, its physical configuration and how it processes the input signal, that is the relationship between input signal and current flowing in the load.

Classification of Signal Amplifier

Type of Signal	Type of Configuration	Classification	Frequency of Operation
Small Signal	Common Emitter	Class A Amplifier	Direct Current (DC)
Large Signal	Common Base	Class B Amplifier	Audio Frequencies (AF)
	Common Collector	Class AB Amplifier	Radio Frequencies (RF)
		Class C Amplifier	VHF, UHF and SHF Frequencies

An ideal signal amplifier will have three main properties: Input Resistance or (R_{IN}), Output Resistance or (R_{OUT}) and of course amplification known commonly as Gain or (A). No matter how complicated an amplifier circuit is, a general amplifier model can still be used to show the relationship of these three properties.

Ideal Amplifier Model

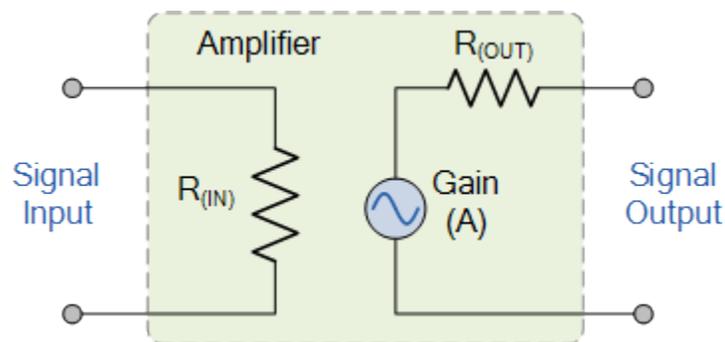

The amplified difference between the input and output signals is known as the Gain of the amplifier. Gain is basically a measure of how much an amplifier “amplifies” the input signal. For example, if we have an input signal of 1 volt and an output of 50 volts, then the gain of the amplifier would be “50”. In other words, the input signal has been increased by a factor of 50. This increase is called **Gain**.


Amplifier gain is simply the ratio of the output divided-by the input. Gain has no units as its a ratio, but in Electronics it is commonly given the symbol “A”, for Amplification. Then the gain of an amplifier is

simply calculated as the “output signal divided by the input signal”.

Amplifier Gain

The introduction to the amplifier gain can be said to be the relationship that exists between the signal measured at the output with the signal measured at the input. There are three different kinds of amplifier gain which can be measured and these are: *Voltage Gain* (A_v), *Current Gain* (A_i) and *Power Gain* (A_p) depending upon the quantity being measured with examples of these different types of gains are given below.

Amplifier Gain of the Input Signal

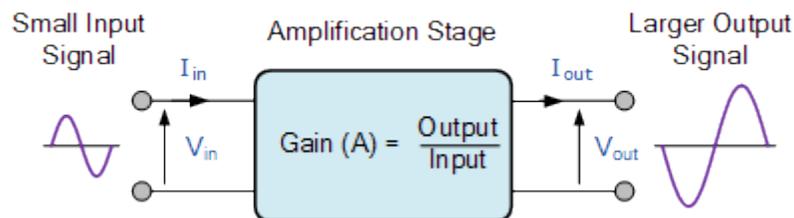

Voltage Amplifier Gain

$$\text{Voltage Gain } (A_v) = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{V_{out}}{V_{in}}$$

Current Amplifier Gain

$$\text{Current Gain } (A_i) = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_{out}}{I_{in}}$$

Power Amplifier Gain

$$\text{Power Gain } (A_p) = A_v \times A_i$$

Note that for the Power Gain you can also divide the power obtained at the output with the power obtained at the input. Also when calculating the gain of an amplifier, the subscripts v, i and p are used to denote the type of signal gain being used.

The power gain (A_p) or power level of the amplifier can also be expressed in **Decibels**, (**dB**). The Bel (B) is a logarithmic unit (base 10) of measurement that has no units. Since the Bel is too large a unit of measure, it is prefixed with *deci* making it **Decibels** instead with one decibel being one tenth (1/10th) of a Bel. To calculate the gain of the amplifier in Decibels or dB, we can use the following expressions.

- Voltage Gain in dB: $a_v = 20 \cdot \log(A_v)$
- Current Gain in dB: $a_i = 20 \cdot \log(A_i)$
- Power Gain in dB: $a_p = 10 \cdot \log(A_p)$

Power Amplifiers

The Small Signal Amplifier is generally referred to as a “Voltage” amplifier because they usually convert a small input voltage into a much larger output

voltage. Sometimes an amplifier circuit is required to drive a motor or feed a loudspeaker and for these types of applications where high switching currents are needed **Power Amplifiers** are required

The power amplifier works on the basic principle of converting the DC power drawn from the power supply into an AC voltage signal delivered to the load. Although the amplification is high the efficiency of the conversion from the DC power supply input to the AC voltage signal output is usually poor.

The perfect or ideal amplifier would give us an efficiency rating of 100% or at least the power “IN” would be equal to the power “OUT”. However, in reality this can never happen as some of the power is lost in the form of heat and also, the amplifier itself consumes power during the amplification process. Then the efficiency of an amplifier is given as:

Amplifier Efficiency

$$\text{Efficiency } (\eta) = \frac{\text{Power delivered to the Load}}{\text{Power taken from the Supply}} = \frac{P_{OUT}}{P_{IN}}$$

Ideal Amplifier

We can now specify the characteristics for an ideal amplifier from our discussion above with regards to its **Gain**, meaning voltage gain:

- The amplifier's gain, (A) should remain constant for varying values of input signal.
- Gain is not affected by frequency. Signals of all frequencies must be amplified by exactly the same amount.
- The amplifier's gain must not add noise to the output signal. It should remove any noise that already exists in the input signal.
- The amplifier's gain should not be affected by changes in temperature giving good temperature stability.
- The gain of the amplifier must remain stable over long periods of time.

Electronic Amplifier Classes

The classification of an amplifier as either a voltage or a power amplifier is made by comparing the characteristics of the input and output signals by measuring the amount of time in relation to the input signal that the current flows in the output circuit.

We saw in the *Common Emitter Transistor* tutorial that for the transistor to operate within its "Active Region" some form of "Base Biasing" was required. This small Base

Bias voltage added to the input signal allowed the transistor to reproduce the full input waveform at its output with no loss of signal.

However, by altering the position of this Base bias voltage, it is possible to operate an amplifier in an amplification mode other than that for full waveform reproduction. With the introduction to the amplifier of a Base bias voltage, different operating ranges and modes of operation can be obtained which are categorized according to their classification. These various mode of operation are better known as **Amplifier Class**.

Audio power amplifiers are classified in an alphabetical order according to their circuit configurations and mode of operation. Amplifiers are designated by different classes of operation such as class "A", class "B", class "C", class "AB", etc. These different amplifier classes range from a near linear output but with low efficiency to a non-linear output but with a high efficiency.

No one class of operation is "better" or "worse" than any other class with the type of operation being determined by the use of the amplifying circuit. There are typical maximum conversion efficiencies for the various types or class of amplifier, with the most commonly used being:

- **Class A Amplifier** – has low efficiency of less than 40% but good signal reproduction and linearity.

- **Class B Amplifier** – is twice as efficient as class A amplifiers with a maximum theoretical efficiency of about 70% because the amplifying device only conducts (and uses power) for half of the input signal.
- **Class AB Amplifier** – has an efficiency rating between that of Class A and Class B but poorer signal reproduction than Class A amplifiers.
- **Class C Amplifier** – is the most efficient amplifier class but distortion is very high as only a small portion of the input signal is amplified therefore the output signal bears very little resemblance to the input signal. Class C amplifiers have the worst signal reproduction