

Marwari college Darbhanga

Subject---physics (Hons)

Class :- B.Sc. part 2

Paper----04 ; Group – B

**Topic--- Basic Electronics (characteristics of BJT in common
Emitter Configuration)**

Lecture series---05

By:- Dr. Sony Kumari,

Assistant professor

Marwari college Darbhanga

Characteristics of BJT in common Emitter Configuration

Characteristics of BJT

Transistors are three terminal active devices made from different semiconductor materials that can act as either an insulator or a conductor by the application of a small signal voltage. The transistor's ability to change between these two states enables it to have two basic functions: "switching" (digital electronics) or "amplification" (analogue electronics). Then bipolar transistors have the ability to operate within three different regions:

- **Active Region** – the transistor operates as an amplifier and $I_c = \beta \cdot I_b$
- **Saturation** – the transistor is "Fully-ON" operating as a switch and $I_c = I(\text{saturation})$
- **Cut-off** – the transistor is "Fully-OFF" operating as a switch and $I_c = 0$

Bipolar Transistor Configurations

As the **Bipolar Transistor** is a three terminal device, there are basically three possible ways to connect it within an electronic circuit with one terminal being common to both the input and output. Each method of connection responding differently to its input signal within a circuit as the static characteristics of the transistor vary with each circuit arrangement.


- Common Base Configuration – has Voltage Gain but no Current Gain.
- Common Emitter Configuration – has both Current and Voltage Gain.
- Common Collector Configuration – has Current Gain but no Voltage Gain.

The Common Emitter (CE) Configuration

In the **Common Emitter** or grounded emitter configuration, the input signal is applied between the base and the emitter, while the output is taken from between the collector and the emitter as shown. This type of configuration is the most commonly used circuit for transistor based amplifiers and which represents the “normal” method of bipolar transistor connection.

The common emitter amplifier configuration produces the highest current and power gain of all the three bipolar transistor configurations. This is mainly because the input impedance is LOW as it is connected to a forward biased PN-junction, while the output impedance is HIGH as it is taken from a reverse biased PN-junction.

The Common Emitter Amplifier Circuit

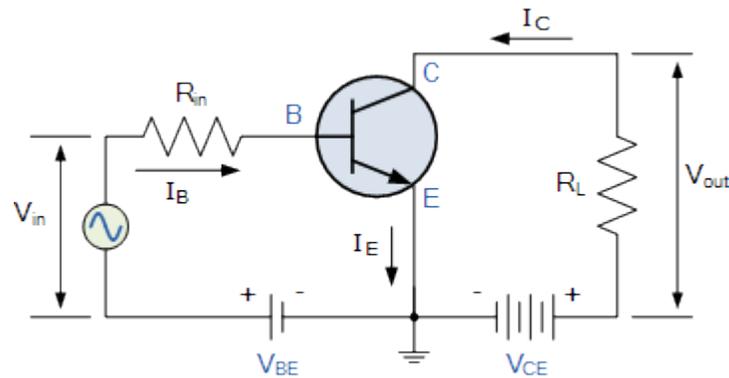

In this type of configuration, the current flowing out of the transistor must be equal to the currents flowing into the transistor as the emitter current is given as $I_E = I_C + I_B$.

As the load resistance (R_L) is connected in series with the collector, the current gain of the common emitter transistor configuration is quite large as it is the ratio of I_C/I_B . A transistor's current gain is given the Greek symbol of Beta, (β).

As the emitter current for a common emitter configuration is defined as $I_E = I_C + I_B$, the ratio of I_C/I_E is called Alpha, given the Greek symbol of α . Note: that the value of Alpha will always be less than unity.

Since the electrical relationship between these three currents, I_B , I_C and I_E is determined by the physical construction of the transistor itself, any small change in the base current (I_B), will result in a much larger change in the collector current (I_C).

Then, small changes in current flowing in the base will thus control the current in the emitter-collector circuit. Typically, Beta has a value between 20 and 200 for most general purpose transistors. So if a transistor has a Beta value of say 100, then one electron will flow from the base terminal for every 100 electrons flowing between the emitter-collector terminal.

By combining the expressions for both Alpha, α and Beta, β the mathematical relationship between these parameters and therefore the current gain of the transistor can be given as:

$$\text{Alpha, } (\alpha) = \frac{I_C}{I_E} \quad \text{and} \quad \text{Beta, } (\beta) = \frac{I_C}{I_B}$$

$$\therefore I_C = \alpha \cdot I_E = \beta \cdot I_B$$

$$\text{as: } \alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$I_E = I_C + I_B$$

Where: “Ic” is the current flowing into the collector terminal, “Ib” is the current flowing into the base terminal and “Ie” is the current flowing out of the emitter terminal.

Then to summarise a little. This type of bipolar transistor configuration has a greater input impedance, current and power gain than that of the common base configuration but its voltage gain is much lower. The common emitter configuration is an inverting amplifier circuit. This means that the resulting output signal has a 180° phase-shift with regards to the input voltage signal.